

# University of New South Wales



## School of Electrical Engineering and Telecommunications

**INDIVIDUAL** Assessment Task: \_\_\_\_\_

|                   |  |             |  |
|-------------------|--|-------------|--|
| Course Code       |  | Course Name |  |
| Week/Session/Year |  | Lecturer    |  |

|                |  |
|----------------|--|
| Student Number |  |
| Family Name    |  |
| Given Names    |  |

**Mark/Grade given (For official use only)**

Marker's Comments:

Since this work counts toward your formal assessment for this course, please write your name and student number where indicated above, and sign the declaration below. Attach this cover sheet to the front of your submission, so that your name and student number can be seen without any cover needing to be opened.

For further information, please see <http://www.lc.unsw.edu.au/plagiarism/index.html>

***I declare that this assessment item is my own work, except where acknowledged, and has not been submitted for academic credit elsewhere, and acknowledge that the assessor of this item may, for the purpose of assessing this item:***

- ***Reproduce this assessment item and provide a copy to another member of the University ; and/or,***
- ***Communicate a copy of this assessment item to a plagiarism checking service (which may then retain a copy of the assessment item on its database for the purpose of future plagiarism checking).***

***I certify that I have read and understood the University Rules in respect of Student Academic Misconduct.***

Signature of student \_\_\_\_\_ Date: \_\_\_\_\_

## ELEC2141 – Assignment 2

### Assumptions

For the design that was implemented, it was assumed that after pressing the start button, the start button would not be pressed a second time until one of two things has occurred:

- The coins have been refunded
- The newspaper has been released

Until one of these has happened, the user will only deposit coins into the system. If the user does press the start button, the state will simply loop to itself, effectively meaning nothing has happened in the overall system.

It is also assumed that the REL and REF signals are handled externally to release the newspaper and refund the inserted coins, respectively.

### State Diagram

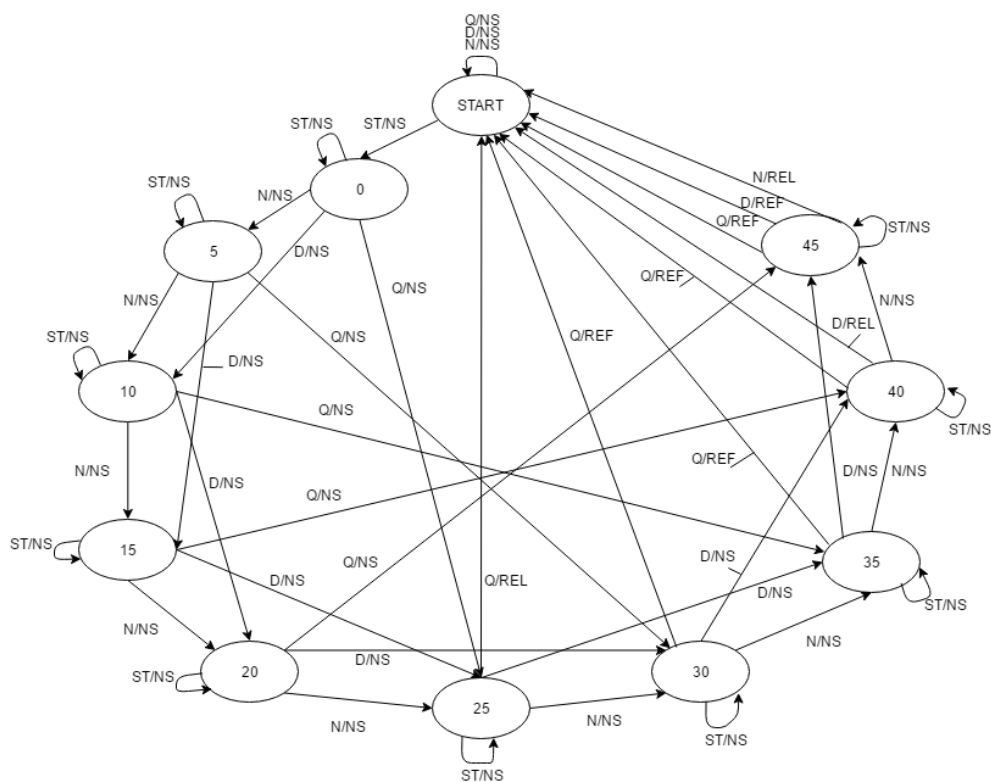


Fig 1. State diagram of the design

The states in the above diagram represent the following:

| State | Meaning   |
|-------|---|
| START | START state, only progresses to next state when START button is pressed |
| 0     | 0c total deposited  |
| 5     | 5c total deposited  |
| 10    | 10c total deposited   |
| 15    | 15c total deposited   |
| 20    | 20c total deposited   |
| 25    | 25c total deposited   |
| 30    | 30c total deposited   |
| 35    | 35c total deposited   |
| 40    | 40c total deposited   |
| 45    | 45c total deposited   |

The table below describes the meaning of the input and outputs:

| Input | Meaning              | Output | Meaning   |
|-------|----------------------|--------|-----------|
| ST    | START button pressed | NS     | No signal |
| N     | Nickel inserted      | REF    | Refund    |
| D     | Dime inserted        | REL    | Release   |
| Q     | Quarter inserted     | -----  | -----     |

Deriving a state table from Fig. 1 yields:

Table 1: State table of the design

| State | Next State |        |        |        | Output  |        |        |        |
|-------|------------|--------|--------|--------|---------|--------|--------|--------|
|       | In = ST    | In = N | In = D | In = Q | In = ST | In = N | In = D | In = Q |
| START | 0          | START  | START  | START  | NS      | NS     | NS     | NS     |
| 0     | 0          | 5      | 10     | 25     | NS      | NS     | NS     | NS     |
| 5     | 5          | 10     | 15     | 30     | NS      | NS     | NS     | NS     |
| 10    | 10         | 15     | 20     | 35     | NS      | NS     | NS     | NS     |
| 15    | 15         | 20     | 25     | 40     | NS      | NS     | NS     | NS     |
| 20    | 20         | 25     | 30     | 45     | NS      | NS     | NS     | NS     |
| 25    | 25         | 30     | 35     | START  | NS      | NS     | NS     | REL    |
| 30    | 30         | 35     | 40     | START  | NS      | NS     | NS     | REF    |
| 35    | 35         | 40     | 45     | START  | NS      | NS     | NS     | REF    |
| 40    | 40         | 45     | START  | START  | NS      | NS     | REL    | REF    |
| 45    | 45         | START  | START  | START  | NS      | REL    | REF    | REF    |

### State minimization

In order to attempt to minimize the number of states, an implication table must be generated from the state table above. The first and second pass of the implication table generation is shown below:

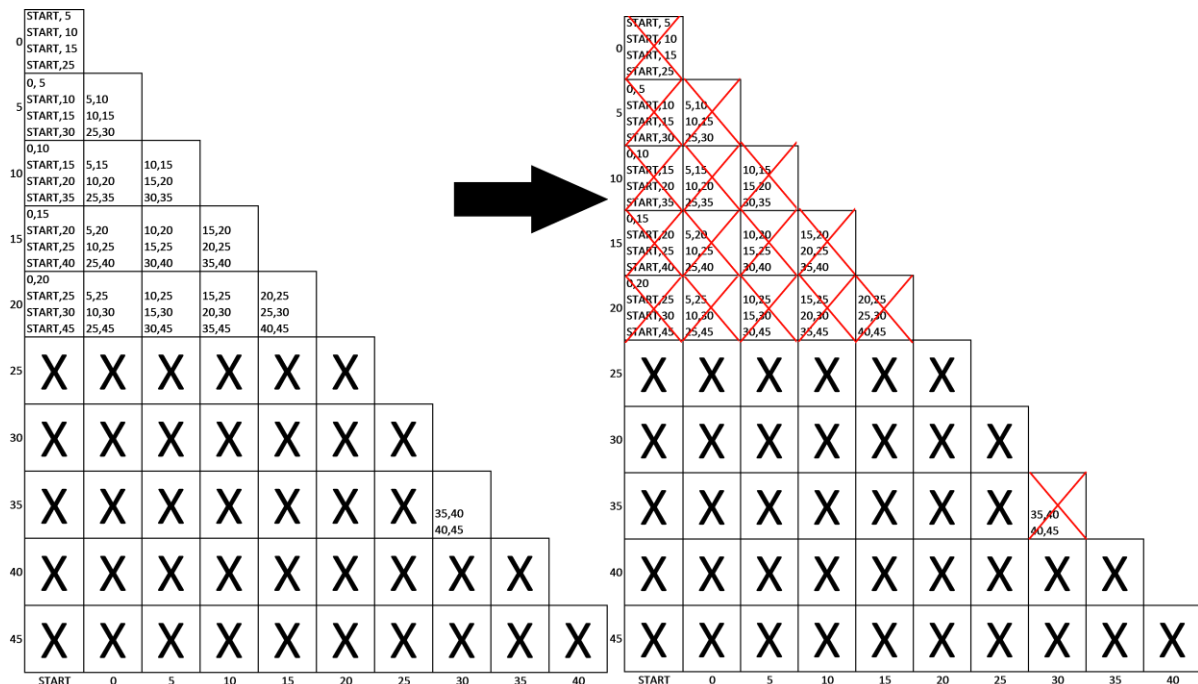


Fig. 2 – Implication table from State table (Table 1)

As can be seen from the above implication table, no state minimization can occur as each state is unique.

## Implementation

The inputs and outputs to the FSM and the states can be assigned as follows (using gray code for the states and regular binary code for the inputs/outputs):

| State | Assignment |
|-------|------------|
| START | 0000       |
| 0     | 0001       |
| 5     | 0011       |
| 10    | 0010       |
| 15    | 0110       |
| 20    | 0111       |
| 25    | 0101       |
| 30    | 0100       |
| 35    | 1100       |
| 40    | 1101       |
| 45    | 1111       |

| Input | Assignment | Output | Assignment |
|-------|------------|--------|------------|
| ST    | 00         | NS     | 00         |
| N     | 01         | REF    | 01         |
| D     | 10         | REL    | 10         |
| Q     | 11         | -----  | -----      |

Redrawing the state table with the new assignments gives the following:

Table 1: State table with state assignments

| State | Next State |         |         |         | Output  |         |         |         |
|-------|------------|---------|---------|---------|---------|---------|---------|---------|
|       | In = 00    | In = 01 | In = 10 | In = 11 | In = 00 | In = 01 | In = 10 | In = 11 |
| 0000  | 0001       | 0000    | 0000    | 0000    | 00      | 00      | 00      | 00      |
| 0001  | 0001       | 0011    | 0010    | 0101    | 00      | 00      | 00      | 00      |
| 0011  | 0011       | 0010    | 0110    | 0100    | 00      | 00      | 00      | 00      |
| 0010  | 0010       | 0110    | 0111    | 1100    | 00      | 00      | 00      | 00      |
| 0110  | 0110       | 0111    | 0101    | 1101    | 00      | 00      | 00      | 00      |
| 0111  | 0111       | 0101    | 0100    | 1111    | 00      | 00      | 00      | 00      |
| 0101  | 0101       | 0100    | 1100    | 0000    | 00      | 00      | 00      | 10      |
| 0100  | 0100       | 1100    | 1101    | 0000    | 00      | 00      | 00      | 01      |
| 1100  | 1100       | 1101    | 1111    | 0000    | 00      | 00      | 00      | 01      |
| 1101  | 1101       | 1111    | 0000    | 0000    | 00      | 00      | 10      | 01      |
| 1111  | 1111       | 0000    | 0000    | 0000    | 00      | 10      | 01      | 01      |

Using the excitation tables for a D flip-flop, T flip-flop and JK flip-flop, the following tables were generated:

| State | D Flip-Flop |         |         |         | T Flip-Flop |         |         |         |
|-------|-------------|---------|---------|---------|-------------|---------|---------|---------|
|       | In = 00     | In = 01 | In = 10 | In = 11 | In = 00     | In = 01 | In = 10 | In = 11 |
| 0000  | 0001        | 0000    | 0000    | 0000    | 0001        | 0000    | 0000    | 0000    |
| 0001  | 0001        | 0011    | 0010    | 0101    | 0000        | 0010    | 0011    | 0100    |
| 0011  | 0011        | 0010    | 0110    | 0100    | 0000        | 0001    | 0101    | 0111    |
| 0010  | 0010        | 0110    | 0111    | 1100    | 0000        | 0100    | 0101    | 1110    |
| 0110  | 0110        | 0111    | 0101    | 1101    | 0000        | 0001    | 0011    | 1011    |
| 0111  | 0111        | 0101    | 0100    | 1111    | 0000        | 0010    | 0011    | 1000    |
| 0101  | 0101        | 0100    | 1100    | 0000    | 0000        | 0001    | 1001    | 0101    |
| 0100  | 0100        | 1100    | 1101    | 0000    | 0000        | 1000    | 1001    | 0100    |
| 1100  | 1100        | 1101    | 1111    | 0000    | 0000        | 0001    | 0011    | 1100    |
| 1101  | 1101        | 1111    | 0000    | 0000    | 0000        | 0010    | 1101    | 1101    |
| 1111  | 1111        | 0000    | 0000    | 0000    | 0000        | 1111    | 1111    | 1111    |

| State | JK Flip-Flop |      |         |      |         |      |         |      |
|-------|--------------|------|---------|------|---------|------|---------|------|
|       | In = 00      |      | In = 01 |      | In = 10 |      | In = 11 |      |
|       | J            | K    | J       | K    | J       | K    | J       | K    |
| 0000  | 0001         | XXXX | 0000    | XXXX | 0000    | XXXX | 0000    | XXXX |
| 0001  | 000X         | XXX0 | 001X    | XXX0 | 001X    | XXX1 | 010X    | XXX0 |
| 0011  | 00XX         | XX00 | 00XX    | XX01 | 01XX    | XX01 | 01XX    | XX11 |
| 0010  | 00X0         | XX0X | 01X0    | XX0X | 01X1    | XX0X | 11X0    | XX1X |
| 0110  | 0XX0         | X00X | 0XX1    | X00X | 0XX1    | X01X | 1XX1    | X01X |
| 0111  | 0XXX         | X000 | 0XXX    | X010 | 0XXX    | X011 | 1XXX    | X000 |
| 0101  | 0X0X         | X0X0 | 0X0X    | X0X1 | 1X0X    | X0X1 | 0X0X    | X1X1 |
| 0100  | 0X00         | X0XX | 1X00    | X0XX | 1X01    | X0XX | 0X00    | X1XX |
| 1100  | XX00         | 00XX | XX01    | 00XX | XX11    | 00XX | XX00    | 11XX |
| 1101  | XX0X         | 00X0 | XX1X    | 00X0 | XX0X    | 11X1 | XX0X    | 11X1 |
| 1111  | XXXX         | 0000 | XXXX    | 1111 | XXXX    | 1111 | XXXX    | 1111 |

The flip-flop input excitation equations were found using 6 variable K-maps assuming the state bits are  $S_3S_2S_1S_0$ , and input bits are  $I_1I_0$ , a K-map was made for each flip-flop for each flip-flop bit ( $D_3D_2D_1D_0$  for D flip-flop,  $T_3T_2T_1T_0$  for T flip-flop  $J_3J_2J_1J_0$  and  $K_3K_2K_1K_0$  for JK flip-flop). So in total, four 6-variable K-maps were required for the D and T flip-flops and eight 6-variable K-maps for the JK flip-flop (4 for J and 4 for K). The output equations had to be found as well in order to draw logic diagrams for each implementation, the output bits were denoted as  $F_1F_0$ .

The Boolean expressions derived from the k-maps were simplified slightly by Boolean factorization. The k-maps are as follows (note that all implicants on the k-maps are essential prime implicants):

## D Flip-flop Inputs

$D_3$

|       |       | $I_1$ |       | $S_0$ |       | $I_1$ |       |
|-------|-------|-------|-------|-------|-------|-------|-------|
|       |       | $I_0$ |       | $I_0$ |       | $I_1$ |       |
| $S_3$ | $S_2$ | $S_1$ | $S_0$ | $S_3$ | $S_2$ | $S_1$ | $S_0$ |
| 0     | 0     | 0     | 0     | 0     | 0     | 0     | 0     |
| 0     | 0     | 1     | 0     | 0     | 0     | 0     | 0     |
| 0     | 0     | 1     | 0     | 0     | 0     | 1     | 0     |
| 0     | 1     | 0     | 1     | 0     | 0     | 0     | 1     |
| X     | X     | X     | X     | X     | X     | X     | X     |
| X     | X     | X     | X     | X     | X     | X     | X     |
| X     | X     | X     | X     | 1     | 0     | 0     | 0     |
| 1     | 1     | 0     | 1     | 1     | 1     | 0     | 0     |

Essential prime implicants:  $S_3\bar{S}_1\bar{I}_1$ ,  $S_3\bar{S}_0\bar{I}_0$ ,  $S_3\bar{I}_1\bar{I}_0$ ,  $S_1\bar{S}_0I_1I_0$ ,  $S_2\bar{S}_1\bar{S}_0\bar{I}_1I_0$ ,  $\bar{S}_3S_2\bar{S}_1I_1\bar{I}_0$ ,  $\bar{S}_3S_2S_1I_1I_0$

$$\therefore D_3 = S_3\bar{S}_1\bar{I}_1 + S_3\bar{S}_0\bar{I}_0 + S_3\bar{I}_1\bar{I}_0 + S_1\bar{S}_0I_1I_0 + S_2\bar{S}_1\bar{S}_0\bar{I}_1I_0 + \bar{S}_3S_2\bar{S}_1I_1\bar{I}_0 + \bar{S}_3S_2S_1I_1I_0$$

$$D_3 = S_3(\bar{S}_1\bar{I}_1 + \bar{I}_0(\bar{S}_0 + \bar{I}_1)) + I_0(\bar{S}_0(S_1I_1 + S_2\bar{S}_1\bar{I}_1)) + \bar{S}_3S_2I_1(S_1 \oplus I_0)$$

$D_2$

|       |       | $I_1$ |       | $S_0$ |       | $I_1$ |       |
|-------|-------|-------|-------|-------|-------|-------|-------|
|       |       | $I_0$ |       | $I_0$ |       | $I_1$ |       |
| $S_3$ | $S_2$ | $S_1$ | $S_0$ | $S_3$ | $S_2$ | $S_1$ | $S_0$ |
| 0     | 0     | 0     | 0     | 0     | 0     | 1     | 0     |
| 0     | 1     | 1     | 1     | 0     | 0     | 1     | 1     |
| 1     | 1     | 1     | 1     | 1     | 1     | 1     | 1     |
| 1     | 1     | 0     | 1     | 1     | 1     | 0     | 1     |
| X     | X     | X     | X     | X     | X     | X     | X     |
| X     | X     | X     | X     | X     | X     | X     | X     |
| X     | X     | X     | X     | 1     | 0     | 0     | 0     |
| 1     | 1     | 0     | 1     | 1     | 1     | 0     | 0     |

Essential prime implicants:  $\bar{S}_3S_1I_1$ ,  $\bar{S}_3S_2\bar{I}_1$ ,  $S_2\bar{S}_1\bar{I}_1$ ,  $\bar{S}_3S_2\bar{I}_0$ ,  $S_1\bar{S}_0I_0$ ,  $S_2\bar{S}_0\bar{I}_0$ ,  $S_2\bar{I}_1\bar{I}_0$ ,  $\bar{S}_2S_0I_1I_0$

$$\therefore D_2 = \bar{S}_3S_1I_1 + \bar{S}_3S_2\bar{I}_1 + S_2\bar{S}_1\bar{I}_1 + \bar{S}_3S_2\bar{I}_0 + S_1\bar{S}_0I_0 + S_2\bar{S}_0\bar{I}_0 + S_2\bar{I}_1\bar{I}_0 + \bar{S}_2S_0I_1I_0$$

$$D_2 = \bar{S}_3(S_1I_1 + S_2(\bar{I}_1 + \bar{I}_0)) + S_2(\bar{S}_1\bar{I}_1 + \bar{I}_0(\bar{S}_0 + \bar{I}_1)) + I_0(\bar{S}_2S_0I_1 + S_1\bar{S}_0)$$

|                |                | I <sub>1</sub> |                |                |                | S <sub>0</sub> |                |                |                |
|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
|                |                | I <sub>0</sub> |                | I <sub>0</sub> |                | I <sub>0</sub> |                | I <sub>0</sub> |                |
|                |                | S <sub>2</sub> | S <sub>1</sub> | S <sub>2</sub> | S <sub>1</sub> | S <sub>2</sub> | S <sub>1</sub> | S <sub>2</sub> | S <sub>1</sub> |
| D <sub>1</sub> | S <sub>3</sub> | 0              | 0              | 0              | 0              | 0              | 1              | 0              | 1              |
|                | S <sub>2</sub> | 1              | 1              | 0              | 1              | 1              | 1              | 0              | 1              |
|                | S <sub>1</sub> | 1              | 1              | 0              | 0              | 1              | 0              | 1              | 0              |
|                | S <sub>0</sub> | 0              | 0              | 0              | 0              | 0              | 0              | 0              | 0              |
| S <sub>3</sub> | S <sub>2</sub> | X              | X              | X              | X              | X              | X              | X              | X              |
|                | S <sub>1</sub> | X              | X              | X              | X              | X              | X              | X              | X              |
|                | S <sub>0</sub> | X              | X              | X              | X              | 1              | 0              | 0              | 0              |
|                | S <sub>3</sub> | 0              | 0              | 0              | 1              | 0              | 1              | 0              | 0              |

Essential prime implicants:  $S_1\bar{S}_0\bar{I}_1$ ,  $\bar{S}_2S_1\bar{I}_0$ ,  $S_1\bar{I}_1\bar{I}_0$ ,  $\bar{S}_2S_0\bar{I}_1I_0$ ,  $\bar{S}_2S_0I_1\bar{I}_0$ ,  $S_3\bar{S}_0I_1\bar{I}_0$ ,  $S_3\bar{S}_1S_0\bar{I}_1I_0$ ,  $\bar{S}_3S_2S_1S_0I_1I_0$

$$\therefore D_1 = S_1\bar{S}_0\bar{I}_1 + \bar{S}_2S_1\bar{I}_0 + S_1\bar{I}_1\bar{I}_0 + \bar{S}_2S_0\bar{I}_1I_0 + \bar{S}_2S_0I_1\bar{I}_0 + S_3\bar{S}_0I_1\bar{I}_0 + S_3\bar{S}_1S_0\bar{I}_1I_0 + \bar{S}_3S_2S_1S_0I_1I_0$$

$$D_1 = S_1(\bar{S}_0\bar{I}_1 + \bar{I}_0(\bar{S}_2 + \bar{I}_1)) + I_1\bar{I}_0(\bar{S}_2S_0 + S_3\bar{S}_0) + S_0I_0(\bar{I}_1(\bar{S}_2 + S_3\bar{S}_1) + \bar{S}_3S_2S_1I_1)$$

|                |                | I <sub>1</sub> |                |                |                | S <sub>0</sub> |                |                |                |
|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
|                |                | I <sub>0</sub> |                | I <sub>0</sub> |                | I <sub>0</sub> |                | I <sub>0</sub> |                |
|                |                | S <sub>2</sub> | S <sub>1</sub> | S <sub>2</sub> | S <sub>1</sub> | S <sub>2</sub> | S <sub>1</sub> | S <sub>2</sub> | S <sub>1</sub> |
| D <sub>0</sub> | S <sub>3</sub> | 1              | 0              | 0              | 0              | 1              | 1              | 1              | 0              |
|                | S <sub>2</sub> | 0              | 0              | 0              | 1              | 1              | 0              | 0              | 0              |
|                | S <sub>1</sub> | 0              | 1              | 1              | 1              | 1              | 1              | 1              | 0              |
|                | S <sub>0</sub> | 0              | 0              | 0              | 1              | 1              | 0              | 0              | 0              |
| S <sub>3</sub> | S <sub>2</sub> | X              | X              | X              | X              | X              | X              | X              | X              |
|                | S <sub>1</sub> | X              | X              | X              | X              | X              | X              | X              | X              |
|                | S <sub>0</sub> | X              | X              | X              | X              | 1              | 0              | 0              | 0              |
|                | S <sub>3</sub> | 0              | 1              | 0              | 1              | 1              | 1              | 0              | 0              |

Essential prime implicants:  $S_0\bar{I}_1\bar{I}_0$ ,  $\bar{S}_3S_2S_1I_0$ ,  $\bar{S}_2\bar{S}_1\bar{I}_1\bar{I}_0$ ,  $\bar{S}_2\bar{S}_1S_0I_0$ ,  $S_1\bar{S}_0I_1\bar{I}_0$ ,  $S_2\bar{S}_0I_1\bar{I}_0$ ,  $S_3\bar{S}_1\bar{I}_1I_0$

$$\therefore D_0 = S_0\bar{I}_1\bar{I}_0 + \bar{S}_3S_2S_1I_0 + \bar{S}_2\bar{S}_1\bar{I}_1\bar{I}_0 + \bar{S}_2\bar{S}_1S_0I_0 + S_1\bar{S}_0I_1\bar{I}_0 + S_2\bar{S}_0I_1\bar{I}_0 + S_3\bar{S}_1\bar{I}_1I_0$$

$$D_0 = \bar{I}_0(S_0\bar{I}_1 + \bar{S}_0I_1(S_1 + S_2)) + \bar{S}_2\bar{S}_1(\bar{I}_1\bar{I}_0 + S_0I_0) + I_0(S_3\bar{S}_1\bar{I}_1 + \bar{S}_3S_2S_1)$$

## T Flip-flop Inputs

|                |                | I <sub>1</sub> |                |                |                | S <sub>0</sub> |                |                |                |
|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
|                |                | I <sub>0</sub> |                | I <sub>0</sub> |                | I <sub>0</sub> |                | I <sub>0</sub> |                |
|                |                | S <sub>2</sub> | S <sub>1</sub> | S <sub>2</sub> | S <sub>1</sub> | S <sub>2</sub> | S <sub>1</sub> | S <sub>2</sub> | S <sub>1</sub> |
| T <sub>3</sub> | S <sub>3</sub> | 0              | 0              | 0              | 0              | 0              | 0              | 0              | 0              |
|                | S <sub>2</sub> | 0              | 0              | 1              | 0              | 0              | 0              | 0              | 0              |
|                | S <sub>1</sub> | 0              | 0              | 1              | 0              | 0              | 0              | 1              | 0              |
|                | S <sub>0</sub> | 0              | 1              | 0              | 1              | 0              | 0              | 0              | 1              |
| S <sub>3</sub> | S <sub>2</sub> | X              | X              | X              | X              | X              | X              | X              | X              |
|                | S <sub>1</sub> | X              | X              | X              | X              | X              | X              | X              | X              |
|                | S <sub>0</sub> | X              | X              | X              | X              | 0              | 1              | 1              | 1              |
|                | S <sub>3</sub> | 0              | 0              | 1              | 0              | 0              | 0              | 1              | 1              |

Essential prime implicants:  $S_3I_1I_0$ ,  $S_3S_0I_1$ ,  $S_3S_1I_0$ ,  $\bar{S}_0I_1I_0$ ,  $S_2S_1I_1I_0$ ,  $\bar{S}_3S_2\bar{S}_1\bar{I}_1\bar{I}_0$ ,  $\bar{S}_3S_2\bar{S}_1\bar{S}_0\bar{I}_1I_0$

$$\therefore T_3 = S_3I_1I_0 + S_3S_0I_1 + S_3S_1I_0 + \bar{S}_0I_1I_0 + S_2S_1I_1I_0 + \bar{S}_3S_2\bar{S}_1\bar{I}_1\bar{I}_0 + \bar{S}_3S_2\bar{S}_1\bar{S}_0\bar{I}_1I_0$$

$$T_3 = S_3(S_0I_1 + S_1I_0) + I_1I_0(S_3 + \bar{S}_0 + S_2S_1) + \bar{S}_3S_2\bar{S}_1(I_1\bar{I}_0 + \bar{S}_0\bar{I}_1I_0)$$

|                |                | I <sub>1</sub> |                |                |                | S <sub>0</sub> |                |                |                |
|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
|                |                | I <sub>0</sub> |                | I <sub>0</sub> |                | I <sub>0</sub> |                | I <sub>0</sub> |                |
|                |                | S <sub>2</sub> | S <sub>1</sub> | S <sub>2</sub> | S <sub>1</sub> | S <sub>2</sub> | S <sub>1</sub> | S <sub>2</sub> | S <sub>1</sub> |
| T <sub>2</sub> | S <sub>3</sub> | 0              | 0              | 0              | 0              | 0              | 0              | 1              | 0              |
|                | S <sub>2</sub> | 0              | 1              | 1              | 1              | 0              | 0              | 1              | 1              |
|                | S <sub>1</sub> | 0              | 0              | 0              | 0              | 0              | 0              | 0              | 0              |
|                | S <sub>0</sub> | 0              | 0              | 1              | 0              | 0              | 0              | 1              | 0              |
| S <sub>3</sub> | S <sub>2</sub> | X              | X              | X              | X              | X              | X              | X              | X              |
|                | S <sub>1</sub> | X              | X              | X              | X              | X              | X              | X              | X              |
|                | S <sub>0</sub> | X              | X              | X              | X              | 0              | 1              | 1              | 1              |
|                | S <sub>3</sub> | 0              | 0              | 1              | 0              | 0              | 0              | 1              | 1              |

Essential prime implicants:  $\bar{S}_2S_1I_1$ ,  $S_3S_0I_1$ ,  $S_3S_1I_0$ ,  $S_2\bar{S}_1I_1I_0$ ,  $\bar{S}_2S_0I_1I_0$ ,  $\bar{S}_2S_1\bar{S}_0I_0$

$$\therefore T_2 = \bar{S}_2S_1I_1 + S_3S_0I_1 + S_3S_1I_0 + S_2\bar{S}_1I_1I_0 + \bar{S}_2S_0I_1I_0 + \bar{S}_2S_1\bar{S}_0I_0$$

$$T_2 = I_1((\bar{S}_2S_1 + S_3S_0) + I_0(S_2\bar{S}_1 + \bar{S}_2S_0)) + S_1I_0(S_3 + \bar{S}_2\bar{S}_0)$$

|                |                | I <sub>1</sub> |                |                |                | S <sub>0</sub> |                |                |                |
|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
|                |                | I <sub>0</sub> |                | I <sub>0</sub> |                | I <sub>0</sub> |                | I <sub>0</sub> |                |
|                |                | S <sub>2</sub> | S <sub>1</sub> | S <sub>2</sub> | S <sub>1</sub> | S <sub>2</sub> | S <sub>1</sub> | S <sub>2</sub> | S <sub>1</sub> |
| T <sub>1</sub> | S <sub>3</sub> | 0              | 0              | 0              | 0              | 0              | 1              | 0              | 1              |
|                | S <sub>2</sub> | 0              | 0              | 1              | 0              | 0              | 0              | 1              | 0              |
|                | S <sub>1</sub> | 0              | 0              | 1              | 1              | 0              | 1              | 0              | 1              |
|                | S <sub>0</sub> | 0              | 0              | 0              | 0              | 0              | 0              | 0              | 0              |
| S <sub>3</sub> | S <sub>2</sub> | X              | X              | X              | X              | X              | X              | X              | X              |
|                | S <sub>1</sub> | X              | X              | X              | X              | X              | X              | X              | X              |
|                | S <sub>0</sub> | X              | X              | X              | X              | 0              | 1              | 1              | 1              |
|                | S <sub>3</sub> | 0              | 0              | 0              | 1              | 0              | 1              | 0              | 0              |

Essential prime implicants:  $S_3S_1I_0$ ,  $\bar{S}_2S_1I_1I_0$ ,  $S_1\bar{S}_0I_1I_0$ ,  $S_2S_1I_1\bar{I}_0$ ,  $S_3\bar{S}_0I_1\bar{I}_0$ ,  $S_3S_0\bar{I}_1I_0$ ,  $S_2S_1S_0\bar{I}_1I_0$ ,  $\bar{S}_2\bar{S}_1S_0\bar{I}_1I_1$ ,  $\bar{S}_2\bar{S}_1S_0I_1\bar{I}_0$

$$\therefore T_1 = S_3S_1I_0 + \bar{S}_2S_1I_1I_0 + S_1\bar{S}_0I_1I_0 + S_2S_1I_1\bar{I}_0 + S_3\bar{S}_0I_1\bar{I}_0 + S_3S_0\bar{I}_1I_0 + S_2S_1S_0\bar{I}_1I_0 + \bar{S}_2\bar{S}_1S_0\bar{I}_1I_1 + \bar{S}_2\bar{S}_1S_0I_1\bar{I}_0$$

$$T_1 = I_0(S_3S_1 + S_0\bar{I}_1(S_3 + \bar{S}_1 \oplus \bar{S}_2)) + I_1(I_0(S_1(\bar{S}_2 + \bar{S}_0)) + \bar{I}_0(S_2S_1 + \bar{S}_2\bar{S}_1S_0 + S_3\bar{S}_0))$$

|                |                | I <sub>1</sub> |                |                |                | S <sub>0</sub> |                |                |                |
|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
|                |                | I <sub>0</sub> |                | I <sub>0</sub> |                | I <sub>0</sub> |                | I <sub>0</sub> |                |
|                |                | S <sub>2</sub> | S <sub>1</sub> | S <sub>2</sub> | S <sub>1</sub> | S <sub>2</sub> | S <sub>1</sub> | S <sub>2</sub> | S <sub>1</sub> |
| T <sub>0</sub> | S <sub>3</sub> | 1              | 0              | 0              | 0              | 0              | 0              | 0              | 1              |
|                | S <sub>2</sub> | 0              | 0              | 0              | 1              | 0              | 1              | 1              | 1              |
|                | S <sub>1</sub> | 0              | 1              | 1              | 1              | 0              | 0              | 0              | 1              |
|                | S <sub>0</sub> | 0              | 0              | 0              | 1              | 0              | 1              | 1              | 1              |
| S <sub>3</sub> | S <sub>2</sub> | X              | X              | X              | X              | X              | X              | X              | X              |
|                | S <sub>1</sub> | X              | X              | X              | X              | X              | X              | X              | X              |
|                | S <sub>0</sub> | X              | X              | X              | X              | 0              | 1              | 1              | 1              |
|                | S <sub>3</sub> | 0              | 1              | 0              | 1              | 0              | 0              | 1              | 1              |

Essential prime implicants:  $S_0I_1\bar{I}_0$ ,  $S_1I_1\bar{I}_0$ ,  $S_2I_1\bar{I}_0$ ,  $S_3S_0I_1$ ,  $S_3S_1I_0$ ,  $\bar{S}_2S_1S_0I_0$ ,  $S_2S_1\bar{S}_0I_0$ ,  $S_3\bar{S}_0\bar{I}_1I_0$ ,  $\bar{S}_3S_2\bar{S}_1S_0I_0$ ,  $\bar{S}_2\bar{S}_1\bar{S}_0\bar{I}_1\bar{I}_0$

$$\therefore T_0 = S_0I_1\bar{I}_0 + S_1I_1\bar{I}_0 + S_2I_1\bar{I}_0 + S_3S_0I_1 + S_3S_1I_0 + \bar{S}_2S_1S_0I_0 + S_2S_1\bar{S}_0I_0 + S_3\bar{S}_0\bar{I}_1I_0 + \bar{S}_3S_2\bar{S}_1S_0I_0 + \bar{S}_2\bar{S}_1\bar{S}_0\bar{I}_1\bar{I}_0$$

$$T_0 = \bar{I}_0(I_1(S_0 + S_1 + S_2) + \bar{S}_0\bar{I}_1(S_3 + \bar{S}_2\bar{S}_1)) + S_1I_0(S_3 + S_0 \oplus S_2) + S_0(\bar{S}_3S_2\bar{S}_1I_0 + S_3I_1)$$

### JK Flip-flop Inputs

|       |               | $S_0$ |       |       |       | $I_1$ |       |       |       |
|-------|---------------|-------|-------|-------|-------|-------|-------|-------|-------|
|       |               | $I_0$ |       | $I_1$ |       | $I_0$ |       | $I_1$ |       |
| $J_3$ | $S_3 S_2 S_1$ | $S_3$ | $S_2$ | $S_1$ | $S_0$ | $I_3$ | $I_2$ | $I_1$ | $I_0$ |
|       | $S_3$         | $S_2$ | $S_1$ | $S_0$ | $I_3$ | $I_2$ | $I_1$ | $I_0$ | $I_0$ |
| $J_3$ | $S_3$         | $S_2$ | $S_1$ | $S_0$ | $I_3$ | $I_2$ | $I_1$ | $I_0$ | $I_0$ |
|       | $S_3$         | $S_2$ | $S_1$ | $S_0$ | $I_3$ | $I_2$ | $I_1$ | $I_0$ | $I_0$ |
|       | $S_3$         | $S_2$ | $S_1$ | $S_0$ | $I_3$ | $I_2$ | $I_1$ | $I_0$ | $I_0$ |
|       | $S_3$         | $S_2$ | $S_1$ | $S_0$ | $I_3$ | $I_2$ | $I_1$ | $I_0$ | $I_0$ |
| $J_3$ | $S_3$         | $S_2$ | $S_1$ | $S_0$ | $I_3$ | $I_2$ | $I_1$ | $I_0$ | $I_0$ |
|       | $S_3$         | $S_2$ | $S_1$ | $S_0$ | $I_3$ | $I_2$ | $I_1$ | $I_0$ | $I_0$ |
|       | $S_3$         | $S_2$ | $S_1$ | $S_0$ | $I_3$ | $I_2$ | $I_1$ | $I_0$ | $I_0$ |
|       | $S_3$         | $S_2$ | $S_1$ | $S_0$ | $I_3$ | $I_2$ | $I_1$ | $I_0$ | $I_0$ |

Essential prime implicants:  $S_1\bar{S}_0I_1I_0$ ,  $S_2\bar{S}_1I_1\bar{I}_0$ ,  $S_2S_1I_1I_0$ ,  $S_2\bar{S}_1\bar{S}_0\bar{I}_1I_0$

$$\therefore J_3 = S_1\bar{S}_0I_1I_0 + S_2\bar{S}_1I_1\bar{I}_0 + S_2S_1I_1I_0 + S_2\bar{S}_1\bar{S}_0\bar{I}_1I_0$$

$$J_3 = I_1I_0(S_1(\bar{S}_0 + S_2)) + S_2\bar{S}_1(I_1\bar{I}_0 + \bar{S}_0\bar{I}_1I_0)$$

|       |               | $S_0$ |       |       |       | $I_1$ |       |       |       |
|-------|---------------|-------|-------|-------|-------|-------|-------|-------|-------|
|       |               | $I_0$ |       | $I_1$ |       | $I_0$ |       | $I_1$ |       |
| $J_2$ | $S_2 S_1 S_0$ | $S_2$ | $S_1$ | $S_0$ | $I_2$ | $I_1$ | $I_0$ | $I_1$ | $I_0$ |
|       | $S_2$         | $S_1$ | $S_0$ | $I_2$ | $I_1$ | $I_0$ | $I_1$ | $I_0$ | $I_0$ |
| $J_2$ | $S_2$         | $S_1$ | $S_0$ | $I_2$ | $I_1$ | $I_0$ | $I_1$ | $I_0$ | $I_0$ |
|       | $S_2$         | $S_1$ | $S_0$ | $I_2$ | $I_1$ | $I_0$ | $I_1$ | $I_0$ | $I_0$ |
|       | $S_2$         | $S_1$ | $S_0$ | $I_2$ | $I_1$ | $I_0$ | $I_1$ | $I_0$ | $I_0$ |
|       | $S_2$         | $S_1$ | $S_0$ | $I_2$ | $I_1$ | $I_0$ | $I_1$ | $I_0$ | $I_0$ |
| $J_2$ | $S_2$         | $S_1$ | $S_0$ | $I_2$ | $I_1$ | $I_0$ | $I_1$ | $I_0$ | $I_0$ |
|       | $S_2$         | $S_1$ | $S_0$ | $I_2$ | $I_1$ | $I_0$ | $I_1$ | $I_0$ | $I_0$ |
|       | $S_2$         | $S_1$ | $S_0$ | $I_2$ | $I_1$ | $I_0$ | $I_1$ | $I_0$ | $I_0$ |
|       | $S_2$         | $S_1$ | $S_0$ | $I_2$ | $I_1$ | $I_0$ | $I_1$ | $I_0$ | $I_0$ |

Essential prime implicants:  $S_1I_1$ ,  $S_0I_1I_0$ ,  $S_1S_0I_0$

$$\therefore J_2 = S_1I_1 + S_0I_1I_0 + S_1S_0I_0$$

$$J_2 = I_1(S_1 + S_0I_0) + S_1S_0I_0$$

|       |               | $S_0$ |       |       |       | $I_1$ |       |       |       |
|-------|---------------|-------|-------|-------|-------|-------|-------|-------|-------|
|       |               | $I_0$ |       | $I_1$ |       | $I_0$ |       | $I_1$ |       |
| $J_1$ | $S_1 S_0 S_2$ | $S_1$ | $S_0$ | $S_2$ | $I_1$ | $I_0$ | $I_1$ | $I_0$ | $I_0$ |
|       | $S_1$         | $S_0$ | $S_2$ | $I_1$ | $I_0$ | $I_1$ | $I_0$ | $I_0$ | $I_0$ |
| $J_1$ | $S_1$         | $S_0$ | $S_2$ | $I_1$ | $I_0$ | $I_1$ | $I_0$ | $I_0$ | $I_0$ |
|       | $S_1$         | $S_0$ | $S_2$ | $I_1$ | $I_0$ | $I_1$ | $I_0$ | $I_0$ | $I_0$ |
|       | $S_1$         | $S_0$ | $S_2$ | $I_1$ | $I_0$ | $I_1$ | $I_0$ | $I_0$ | $I_0$ |
|       | $S_1$         | $S_0$ | $S_2$ | $I_1$ | $I_0$ | $I_1$ | $I_0$ | $I_0$ | $I_0$ |
| $J_1$ | $S_1$         | $S_0$ | $S_2$ | $I_1$ | $I_0$ | $I_1$ | $I_0$ | $I_0$ | $I_0$ |
|       | $S_1$         | $S_0$ | $S_2$ | $I_1$ | $I_0$ | $I_1$ | $I_0$ | $I_0$ | $I_0$ |
|       | $S_1$         | $S_0$ | $S_2$ | $I_1$ | $I_0$ | $I_1$ | $I_0$ | $I_0$ | $I_0$ |
|       | $S_1$         | $S_0$ | $S_2$ | $I_1$ | $I_0$ | $I_1$ | $I_0$ | $I_0$ | $I_0$ |

Essential prime implicants:  $\bar{S}_2S_0I_1I_0$ ,  $\bar{S}_2S_0I_1\bar{I}_0$ ,  $S_3\bar{S}_0I_1\bar{I}_0$ ,  $S_3S_0\bar{I}_1I_0$

$$\therefore J_1 = \bar{S}_2S_0I_1I_0 + \bar{S}_2S_0I_1\bar{I}_0 + S_3\bar{S}_0I_1\bar{I}_0 + S_3S_0\bar{I}_1I_0$$

$$J_1 = \bar{S}_2S_0(I_0 \oplus I_1) + S_3(\bar{S}_0I_1\bar{I}_0 + S_0\bar{I}_1I_0)$$

|       |               | $S_0$ |       |       |       | $I_1$ |       |       |       |
|-------|---------------|-------|-------|-------|-------|-------|-------|-------|-------|
|       |               | $I_0$ |       | $I_1$ |       | $I_0$ |       | $I_1$ |       |
| $J_0$ | $S_0 S_1 S_2$ | $S_0$ | $S_1$ | $S_2$ | $I_0$ | $I_1$ | $I_0$ | $I_1$ | $I_0$ |
|       | $S_0$         | $S_1$ | $S_2$ | $I_0$ | $I_1$ | $I_0$ | $I_1$ | $I_0$ | $I_0$ |
| $J_0$ | $S_0$         | $S_1$ | $S_2$ | $I_0$ | $I_1$ | $I_0$ | $I_1$ | $I_0$ | $I_0$ |
|       | $S_0$         | $S_1$ | $S_2$ | $I_0$ | $I_1$ | $I_0$ | $I_1$ | $I_0$ | $I_0$ |
|       | $S_0$         | $S_1$ | $S_2$ | $I_0$ | $I_1$ | $I_0$ | $I_1$ | $I_0$ | $I_0$ |
|       | $S_0$         | $S_1$ | $S_2$ | $I_0$ | $I_1$ | $I_0$ | $I_1$ | $I_0$ | $I_0$ |
| $J_0$ | $S_0$         | $S_1$ | $S_2$ | $I_0$ | $I_1$ | $I_0$ | $I_1$ | $I_0$ | $I_0$ |
|       | $S_0$         | $S_1$ | $S_2$ | $I_0$ | $I_1$ | $I_0$ | $I_1$ | $I_0$ | $I_0$ |
|       | $S_0$         | $S_1$ | $S_2$ | $I_0$ | $I_1$ | $I_0$ | $I_1$ | $I_0$ | $I_0$ |
|       | $S_0$         | $S_1$ | $S_2$ | $I_0$ | $I_1$ | $I_0$ | $I_1$ | $I_0$ | $I_0$ |

Essential prime implicants:  $S_1I_1\bar{I}_0$ ,  $S_2I_1\bar{I}_0$ ,  $S_2S_1I_0$ ,  $S_3\bar{I}_1I_0$ ,  $\bar{S}_2\bar{S}_1\bar{I}_1\bar{I}_0$

$$\therefore J_0 = S_1I_1\bar{I}_0 + S_2I_1\bar{I}_0 + S_2S_1I_0 + S_3\bar{I}_1I_0 + \bar{S}_2\bar{S}_1\bar{I}_1\bar{I}_0$$

$$J_0 = \bar{I}_0(I_1(S_1 + S_2) + \bar{S}_2\bar{S}_1\bar{I}_1) + I_0(S_2S_1 + S_3\bar{I}_1)$$

|       |               | $S_0$ |       |       |       | $I_1$ |       |       |       |
|-------|---------------|-------|-------|-------|-------|-------|-------|-------|-------|
|       |               | $I_0$ |       | $I_1$ |       | $I_0$ |       | $I_1$ |       |
| $K_3$ | $S_3 S_2 S_1$ | $S_3$ | $S_2$ | $S_1$ | $I_3$ | $I_2$ | $I_1$ | $I_0$ | $I_0$ |
|       | $S_3$         | $S_2$ | $S_1$ | $S_0$ | $I_3$ | $I_2$ | $I_1$ | $I_0$ | $I_0$ |
| $K_3$ | $S_3$         | $S_2$ | $S_1$ | $I_3$ | $I_2$ | $I_1$ | $I_0$ | $I_0$ | $I_0$ |
|       | $S_3$         | $S_2$ | $S_1$ | $I_3$ | $I_2$ | $I_1$ | $I_0$ | $I_0$ | $I_0$ |
|       | $S_3$         | $S_2$ | $S_1$ | $I_3$ | $I_2$ | $I_1$ | $I_0$ | $I_0$ | $I_0$ |
|       | $S_3$         | $S_2$ | $S_1$ | $I_3$ | $I_2$ | $I_1$ | $I_0$ | $I_0$ | $I_0$ |
| $K_3$ | $S_3$         | $S_2$ | $S_1$ | $I_3$ | $I_2$ | $I_1$ | $I_0$ | $I_0$ | $I_0$ |
|       | $S_3$         | $S_2$ | $S_1$ | $I_3$ | $I_2$ | $I_1$ | $I_0$ | $I_0$ | $I_0$ |
|       | $S_3$         | $S_2$ | $S_1$ | $I_3$ | $I_2$ | $I_1$ | $I_0$ | $I_0$ | $I_0$ |
|       | $S_3$         | $S_2$ | $S_1$ | $I_3$ | $I_2$ | $I_1$ | $I_0$ | $I_0$ | $I_0$ |

Essential prime implicants:  $I_1I_0$ ,  $S_0I_1$ ,  $S_1I_0$

$$\therefore K_3 = I_1I_0 + S_0I_1 + S_1I_0$$

$$K_3 = I_0(I_1 + S_1) + S_0I_1$$

|       |               | $S_0$ |       |       |       | $I_1$ |       |       |       |
|-------|---------------|-------|-------|-------|-------|-------|-------|-------|-------|
|       |               | $I_0$ |       | $I_1$ |       | $I_0$ |       | $I_1$ |       |
| $K_2$ | $S_2 S_1 S_0$ | $S_2$ | $S_1$ | $S_0$ | $I_2$ | $I_1$ | $I_0$ | $I_1$ | $I_0$ |
|       | $S_2$         | $S_1$ | $S_0$ | $I_2$ | $I_1$ | $I_0$ | $I_1$ | $I_0$ | $I_0$ |
| $K_2$ | $S_2$         | $S_1$ | $S_0$ | $I_2$ | $I_1$ | $I_0$ | $I_1$ | $I_0$ | $I_0$ |
|       | $S_2$         | $S_1$ | $S_0$ | $I_2$ | $I_1$ | $I_0$ | $I_1$ | $I_0$ | $I_0$ |
|       | $S_2$         | $S_1$ | $S_0$ | $I_2$ | $I_1$ | $I_0$ | $I_1$ | $I_0$ | $I_0$ |
|       | $S_2$         | $S_1$ | $S_0$ | $I_2$ | $I_1$ | $I_0$ | $I_1$ | $I_0$ | $I_0$ |
| $K_2$ | $S_2$         | $S_1$ | $S_0$ | $I_2$ | $I_1$ | $I_0$ | $I_1$ | $I_0$ | $I_0$ |
|       | $S_2$         | $S_1$ | $S_0$ | $I_2$ | $I_1$ | $I_0$ | $I_1$ | $I_0$ | $I_0$ |
|       | $S_2$         | $S_1$ | $S_0$ | $I_2$ | $I_1$ | $I_0$ | $I_1$ | $I_0$ | $I_0$ |
|       | $S_2$         | $S_1$ | $S_0$ | $I_2$ | $I_1$ | $I_0$ | $I_1$ | $I_0$ | $I_0$ |

Essential prime implicants:  $\bar{S}_1I_1I_0$ ,  $S_3S_0I_1$ ,  $S_3S_1I_0$

$$\therefore K_2 = \bar{S}_1I_1I_0 + S_3S_0I_1 + S_3S_1I_0$$

$$K_2 = I_1(\bar{S}_1I_0 + S_3S_0) + S_3S_1I_0$$

|       |       | $S_0$ |   |       |   | $S_1$ |   |       |   |
|-------|-------|-------|---|-------|---|-------|---|-------|---|
|       |       | $I_0$ |   | $I_1$ |   | $I_0$ |   | $I_1$ |   |
| $K_1$ | $S_3$ | X     | X | X     | X | X     | X | X     | X |
|       | $S_2$ | 0     | 0 | 1     | 0 | 0     | 0 | 1     | 0 |
|       | $S_1$ | 0     | 0 | 1     | 1 | 0     | 1 | 0     | 1 |
|       | $S_0$ | X     | X | X     | X | X     | X | X     | X |
|       | $S_3$ | X     | X | X     | X | X     | X | X     | X |
|       | $S_2$ | X     | X | X     | X | 0     | 1 | 1     | 1 |
|       | $S_1$ | X     | X | X     | X | 0     | 1 | 1     | 1 |
|       | $S_0$ | X     | X | X     | X | X     | X | X     | X |

Essential prime implicants:  $S_3I_0$ ,  $\bar{S}_2I_1I_0$ ,  $\bar{S}_0I_1I_0$ ,  $S_2I_1\bar{I}_0$ ,  $S_2S_0\bar{I}_1I_0$

$$\therefore K_1 = S_3I_0 + \bar{S}_2I_1I_0 + \bar{S}_0I_1I_0 + S_2I_1\bar{I}_0 + S_2S_0\bar{I}_1I_0$$

$$K_1 = I_0(S_3 + I_1(\bar{S}_2 + \bar{S}_0) + S_2I_1\bar{I}_0) + S_2I_1\bar{I}_0$$

|       |       | $S_0$ |   |       |   | $S_1$ |   |       |   |
|-------|-------|-------|---|-------|---|-------|---|-------|---|
|       |       | $I_0$ |   | $I_1$ |   | $I_0$ |   | $I_1$ |   |
| $K_0$ | $S_3$ | X     | X | X     | X | 0     | 0 | 0     | 1 |
|       | $S_2$ | X     | X | X     | X | 0     | 1 | 1     | 1 |
|       | $S_1$ | X     | X | X     | X | 0     | 0 | 0     | 1 |
|       | $S_0$ | X     | X | X     | X | 0     | 1 | 1     | 1 |
|       | $S_3$ | X     | X | X     | X | X     | X | X     | X |
|       | $S_2$ | X     | X | X     | X | X     | X | X     | X |
|       | $S_1$ | X     | X | X     | X | 0     | 1 | 1     | 1 |
|       | $S_0$ | X     | X | X     | X | 0     | 0 | 1     | 1 |

Essential prime implicants:  $I_1\bar{I}_0$ ,  $S_3I_1$ ,  $\bar{S}_2S_1I_0$ ,  $S_3S_1I_0$ ,  $\bar{S}_3S_2\bar{S}_1I_0$

$$\therefore K_0 = I_1\bar{I}_0 + S_3I_1 + \bar{S}_2S_1I_0 + S_3S_1I_0 + \bar{S}_3S_2\bar{S}_1I_0$$

$$K_0 = I_1\bar{I}_0 + S_3I_1 + I_0(S_1(\bar{S}_2 + S_3) + \bar{S}_3S_2\bar{S}_1)$$

## Outputs

|       |       | $S_0$ |   |       |   | $S_1$ |   |       |   |
|-------|-------|-------|---|-------|---|-------|---|-------|---|
|       |       | $I_0$ |   | $I_1$ |   | $I_0$ |   | $I_1$ |   |
| $F_1$ | $S_3$ | 0     | 0 | 0     | 0 | 0     | 0 | 0     | 0 |
|       | $S_2$ | 0     | 0 | 0     | 0 | 0     | 0 | 0     | 0 |
|       | $S_1$ | 0     | 0 | 0     | 0 | 0     | 0 | 0     | 0 |
|       | $S_0$ | 0     | 0 | 0     | 0 | 0     | 0 | 1     | 0 |
|       | $S_3$ | X     | X | X     | X | X     | X | X     | X |
|       | $S_2$ | X     | X | X     | X | X     | X | X     | X |
|       | $S_1$ | X     | X | X     | X | 0     | 1 | 0     | 0 |
|       | $S_0$ | 0     | 0 | 0     | 0 | 0     | 0 | 0     | 1 |

Essential prime implicants:  $S_3S_1\bar{I}_1I_0$ ,  $S_3\bar{S}_1S_0I_1\bar{I}_0$ ,  $\bar{S}_3S_2\bar{S}_1S_0I_1I_0$

$$\therefore F_1 = S_3S_1\bar{I}_1I_0 + S_3\bar{S}_1S_0I_1\bar{I}_0 + \bar{S}_3S_2\bar{S}_1S_0I_1I_0$$

$$F_1 = S_3S_1\bar{I}_1I_0 + S_0I_1(S_3\bar{S}_1\bar{I}_0 + \bar{S}_3S_2\bar{S}_1I_0)$$

|       |       | $S_0$ |   |       |   | $S_1$ |   |       |   |
|-------|-------|-------|---|-------|---|-------|---|-------|---|
|       |       | $I_0$ |   | $I_1$ |   | $I_0$ |   | $I_1$ |   |
| $F_0$ | $S_3$ | 0     | 0 | 0     | 0 | 0     | 0 | 0     | 0 |
|       | $S_2$ | 0     | 0 | 0     | 0 | 0     | 0 | 0     | 0 |
|       | $S_1$ | 0     | 0 | 0     | 0 | 0     | 0 | 0     | 0 |
|       | $S_0$ | 0     | 0 | 1     | 0 | 0     | 0 | 0     | 0 |
|       | $S_3$ | X     | X | X     | X | X     | X | X     | X |
|       | $S_2$ | X     | X | X     | X | X     | X | X     | X |
|       | $S_1$ | X     | X | X     | X | 0     | 0 | 1     | 1 |
|       | $S_0$ | 0     | 0 | 1     | 0 | 0     | 0 | 1     | 0 |

Essential prime implicants:  $S_3I_1I_0$ ,  $S_3S_1I_1$ ,  $S_2\bar{S}_1\bar{S}_0I_1I_0$

$$\therefore F_0 = S_3I_1I_0 + S_3S_1I_1 + S_2\bar{S}_1\bar{S}_0I_1I_0$$

$$F_0 = I_1(S_3(I_0 + S_1) + S_2\bar{S}_1\bar{S}_0I_0)$$

From the above Boolean expression derivations, the logic diagrams for each implementation (D, T and JK implementations) can be drawn (note that most wires were omitted and replaced with labels in order to preserve readability of the diagrams, also the flip-flops were assumed to have an active-low clear input, hence why they are connected to Vcc). The labels are assigned to mean the following:

| Label    | Meaning                         |
|----------|---------------------------------|
| X NOT    | The complement of some signal X |
| IN_1/0   | The input bits                  |
| F1/0     | The output bits                 |
| S3/2/1/0 | State bits                      |



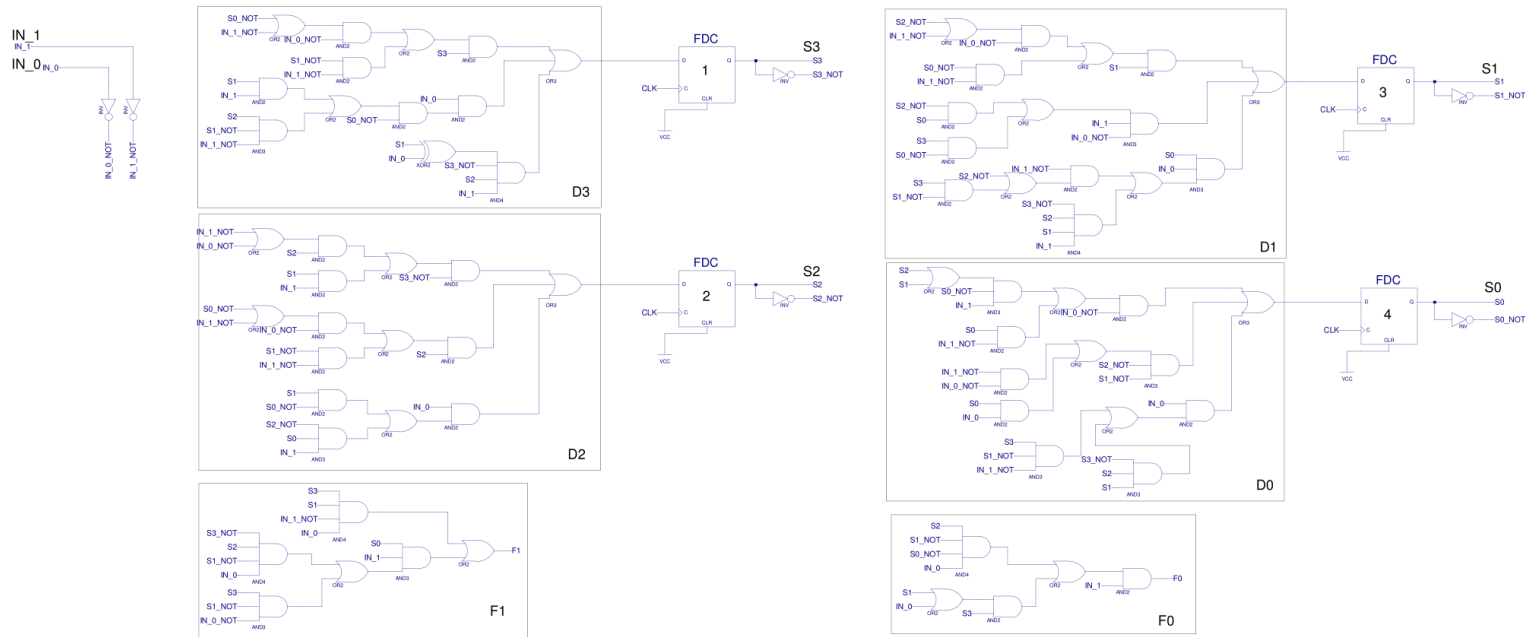


Fig. 3 – D flip-flop implementation of design

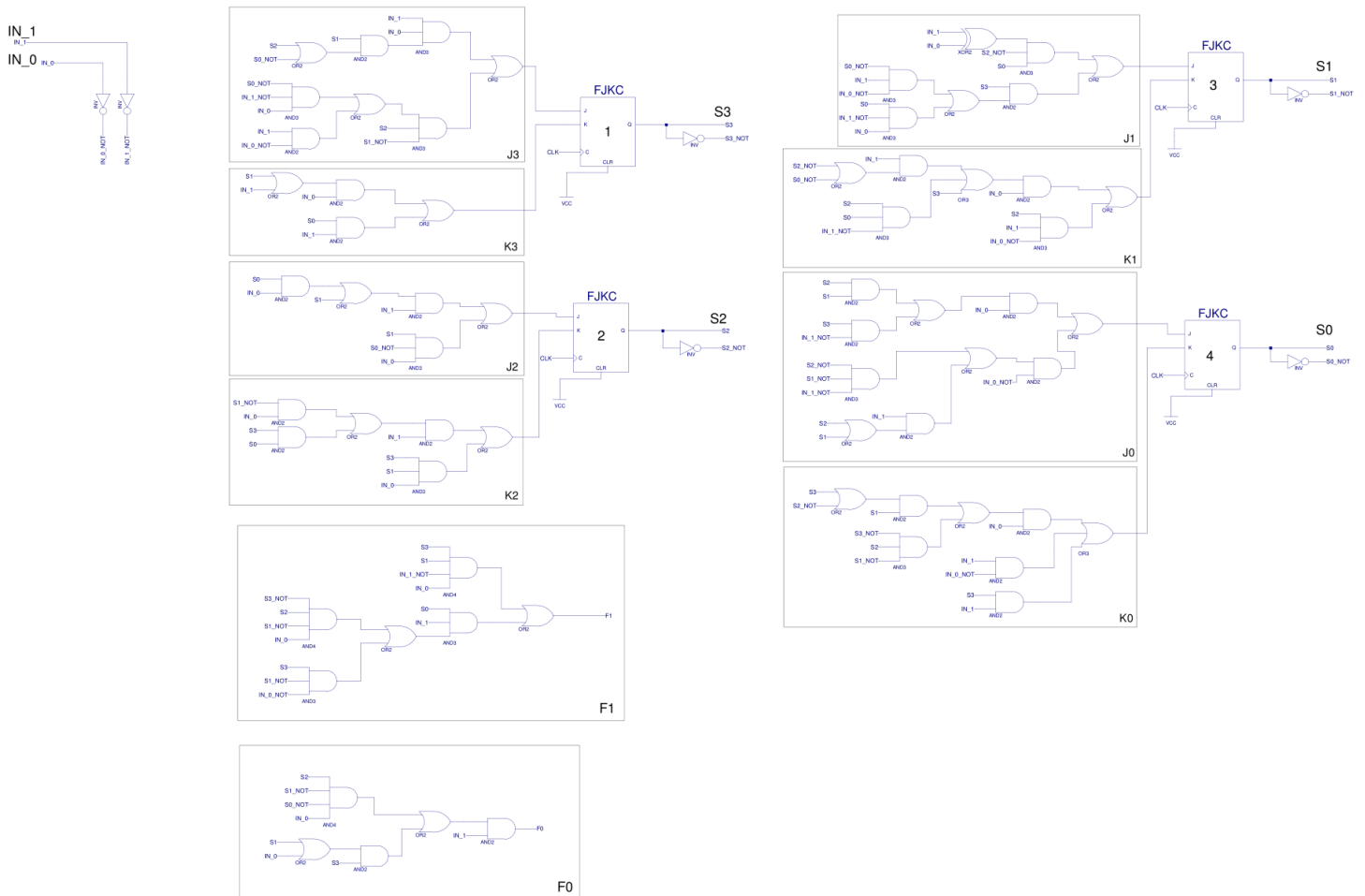


Fig. 4 – JK flip-flop implementation of design

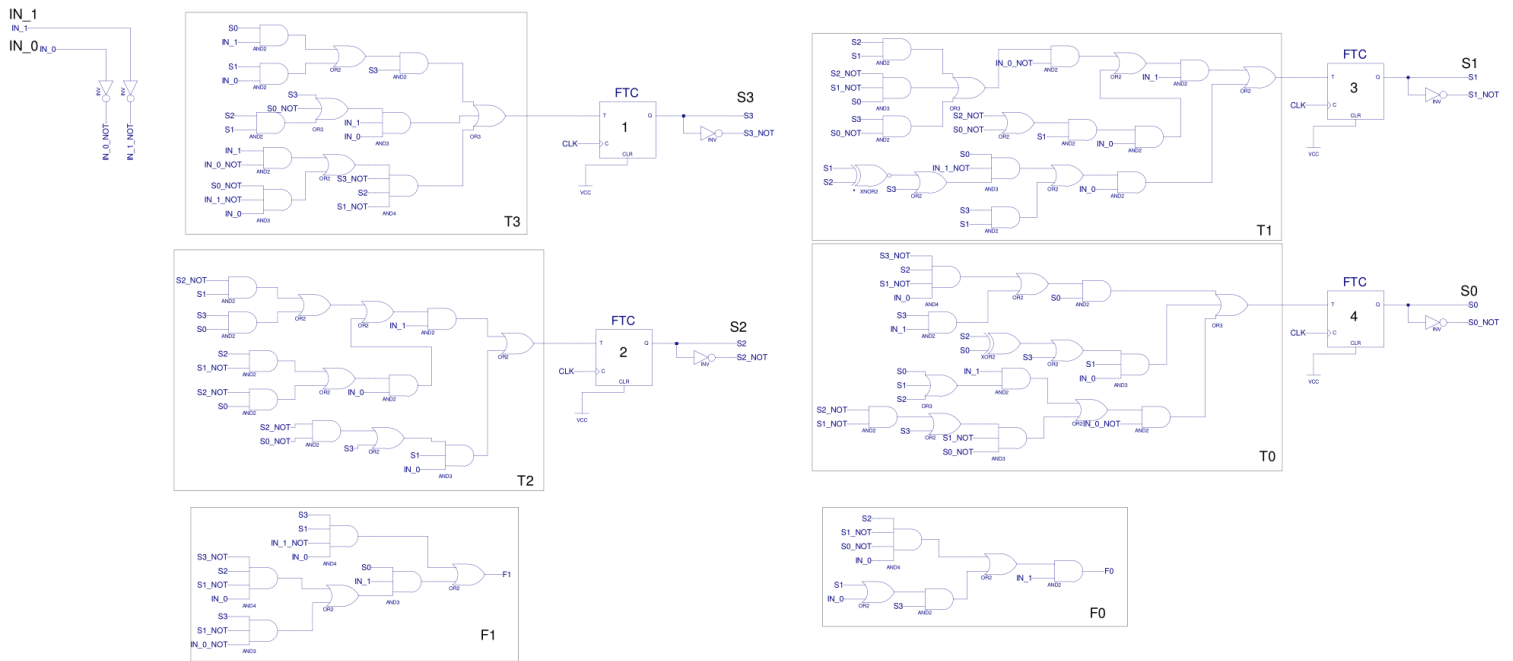


Fig. 5 – T flip-flop implementation of design

## Gate input cost

By simply counting the gates in the above logic diagrams, the GIC for the inputs into the flip-flops and outputs of each implementation was found. An assumption was made that the flip-flops used didn't have a "free" complement of the output from the flip-flop and instead had to be manually inverted, adding a GIC of 4 (GIC(State inverters) = 4) to each implementation. It was also assumed that XOR/XNOR gates had a GIC of 2, and that the flip-flops themselves did not have a clear (it is not used in this implementation and so in real application a flip-flop without clear would be used in it's place), therefore the flip-flops had GICs of:

$$\text{GIC(D FF)} = 9, \text{GIC(T FF)} = 10, \text{GIC(JK FF)} = 10$$

The output circuit and inputs are common to all implementations and they have a GIC of:

$$\text{GIC}(F_1) = 18, \text{GIC}(F_0) = 12, \text{GIC}(\text{Input}) = 2$$

## D Flip-flop implementation

$$\text{GIC}(D_3) = 30, \text{GIC}(D_2) = 32, \text{GIC}(D_1) = 37, \text{GIC}(D_0) = 33$$

So the GIC of the flip-flop input equations and outputs is:

$$\text{GIC}(D_3) + \text{GIC}(D_2) + \text{GIC}(D_1) + \text{GIC}(D_0) + \text{GIC}(F_1) + \text{GIC}(F_0) + \text{GIC}(\text{Input}) + \text{GIC}(\text{State inverters}) + 4 \times \text{GIC}(\text{D FF})$$

$$= 204$$

## T Flip-flop implementation

$$\text{GIC}(T_3) = 30, \text{GIC}(T_2) = 27, \text{GIC}(T_1) = 37, \text{GIC}(T_0) = 36$$

So the GIC of the flip-flop input equations and outputs is:

$$\text{GIC}(T_3) + \text{GIC}(T_2) + \text{GIC}(T_1) + \text{GIC}(T_0) + \text{GIC}(F_1) + \text{GIC}(F_0) + \text{GIC}(\text{Input}) + \text{GIC}(\text{State inverters}) + 4 \times \text{GIC}(\text{T FF})$$

$$= 206$$

Zachary Hamid  
z5059915

### JK Flip-flop implementation

$GIC(J_3) = 19$ ,  $GIC(J_2) = 11$ ,  $GIC(J_1) = 17$ ,  $GIC(J_0) = 21$ ,  $GIC(K_3) = 8$ ,  $GIC(K_2) = 13$ ,  $GIC(K_1) = 17$ ,  
 $GIC(K_0) = 18$

So the GIC of the flip-flop input equations and outputs is:

$GIC(J_3) + GIC(J_2) + GIC(J_1) + GIC(J_0) + GIC(K_3) + GIC(K_2) + GIC(K_1) + GIC(K_0) + GIC(F_1) + GIC(F_0)$   
 $+ GIC(\text{Input}) + GIC(\text{State inverters}) + 4 \times GIC(\text{JK FF})$

$= 200$

So, it can be seen that the GIC of each circuit is incredibly similar, with JK being the most optimal implementation by a small margin (however, the original Boolean expressions may not have been completely optimally reduced and so this result could change, since the difference in GIC between implementations is so small). Since the gate input costs are only marginally different, it doesn't particularly matter which implementation is chosen for this design, however JK flip-flops have 8 less complex sub-circuits and so have more modularity than the other designs.

## Verification

The schematics for the D implementation in Xilinx can be seen above in Implementation. This implementation was tested using the behavioural Verilog HDL rather than using the schematic. The test bench is shown below, the input was set as always having nickels inserted into the system with a start signal input to go from state START -> 0c, and it sequentially goes through each state.

```
1  `timescale 1ns / 1ps
2  module beh_tbw;
3
4      // Inputs
5      reg [1:0] IN;
6      reg CLK;
7
8      // Outputs
9      wire [1:0] OUT;
10     wire [3:0] state;
11     wire [3:0] next_state;
12
13     // Instantiate the Unit Under Test (UUT)
14     DFF_Beh uut (
15         .IN(IN),
16         .CLK(CLK),
17         .OUT(OUT),
18         .state(state),
19         .next_state(next_state)
20     );
21
22     initial begin
23         // Initialize Inputs
24         IN = 2'b00;
25         CLK = 1'b0;
26
27         // Wait 100 ns for global reset to finish
28         #100; // Hold clock off for 100ns so 0000 state stays on for same time as the
other states
29         #100;
30         CLK = ~CLK;
31         #100;
32         CLK = ~CLK;
33         IN = 2'b01; //After initial input of 00 to go from START -> 0c states, input
nickels, this ensures every state is visited
//sequentially
34         forever
35         begin
36             #100;
37             CLK = ~CLK; //alternate clock every 100ns
38         end
39     end
40 end
41
42 endmodule
```

Fig. 6 – Test bench for verification of the D implementation of the FSM

This test bench produced the following simulation:

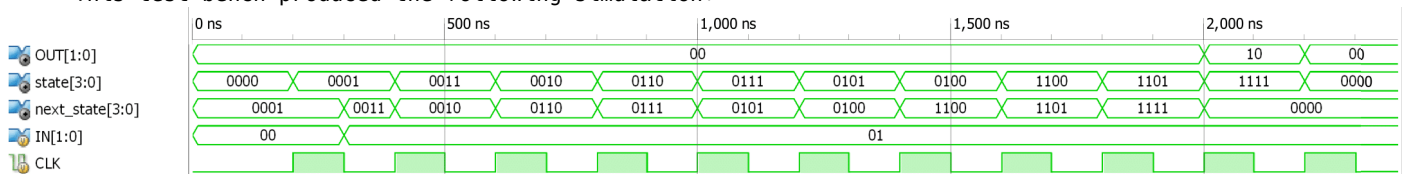


Fig. 7 – Simulation output for all nickel input (excl. initial input START)

By changing line 33 in the test bench to give a different constant input of dimes and quarters these simulations were generated:

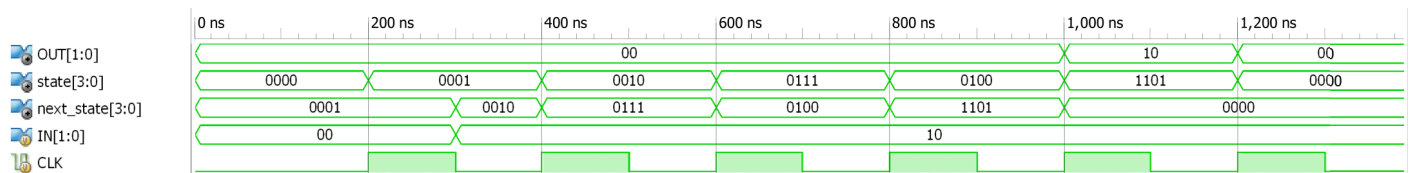


Fig. 8 – Simulation output for all dime input (excl. initial input START)

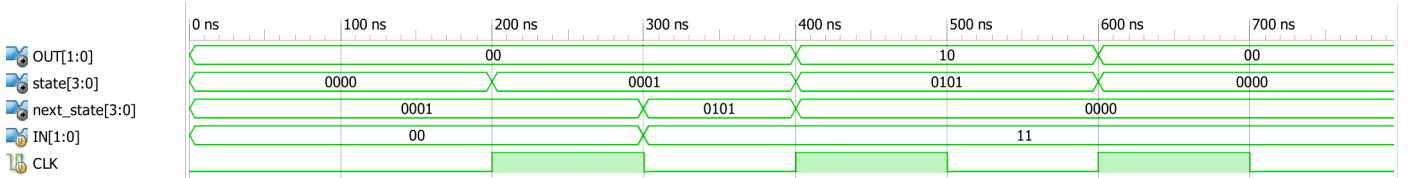


Fig. 9 – Simulation output for all quarter input (excl. initial input START)

## Verilog HDL

The behavioural Verilog HDL that was used to verify the D implementation of the design is shown below:

```
1  `timescale 1ns / 1ps
2  module DFF_Beh(
3      input [1:0] IN,
4      input CLK,
5      output reg [1:0] OUT,
6      output reg [3:0] state, next_state
7  );
8      // Possible states
9      parameter S0 = 4'b0000, S1 = 4'b0001, S2 = 4'b0011, S3 = 4'b0010,
10         S4 = 4'b0110, S5 = 4'b0111, S6 = 4'b0101, S7 = 4'b0100,
11         S8 = 4'b1100, S9 = 4'b1101, S10 = 4'b1111;
12      //Possible inputs
13      parameter I0 = 2'b00, I1 = 2'b01, I2 = 2'b10, I3 = 2'b11;
14      //Possible outputs
15      parameter NS = 2'b00, REF = 2'b01, REL = 2'b10;
16      initial state = S0;
17      initial next_state = S0;
18      initial OUT = NS;
19      always @(posedge CLK)
20          state <= next_state;
21      always @(state, IN)
22          case(state)
23              S0: case (IN)
24                  I0: next_state <= S1;
25                  I1: next_state <= S0;
26                  I2: next_state <= S0;
27                  I3: next_state <= S0;
28              endcase
29              S1: case (IN)
30                  I0: next_state <= S1;
31                  I1: next_state <= S2;
32                  I2: next_state <= S3;
33                  I3: next_state <= S6;
34              endcase
35              S2: case (IN)
36                  I0: next_state <= S2;
37                  I1: next_state <= S3;
38                  I2: next_state <= S4;
39                  I3: next_state <= S7;
40              endcase
41              S3: case (IN)
42                  I0: next_state <= S3;
43                  I1: next_state <= S4;
44                  I2: next_state <= S5;
45                  I3: next_state <= S8;
46              endcase
47              S4: case (IN)
48                  I0: next_state <= S4;
49                  I1: next_state <= S5;
50                  I2: next_state <= S6;
51                  I3: next_state <= S9;
52              endcase
53              S5: case (IN)
54                  I0: next_state <= S5;
55                  I1: next_state <= S6;
56                  I2: next_state <= S7;
57                  I3: next_state <= S10;
```

```
58         endcase
59     S6: case (IN)
60         I0: next_state <= S6;
61         I1: next_state <= S7;
62         I2: next_state <= S8;
63         I3: next_state <= S0;
64     endcase
65     S7: case (IN)
66         I0: next_state <= S7;
67         I1: next_state <= S8;
68         I2: next_state <= S9;
69         I3: next_state <= S0;
70     endcase
71     S8: case (IN)
72         I0: next_state <= S8;
73         I1: next_state <= S9;
74         I2: next_state <= S10;
75         I3: next_state <= S0;
76     endcase
77     S9: case (IN)
78         I0: next_state <= S9;
79         I1: next_state <= S10;
80         I2: next_state <= S0;
81         I3: next_state <= S0;
82     endcase
83     S10: case (IN)
84         I0: next_state <= S10;
85         I1: next_state <= S0;
86         I2: next_state <= S0;
87         I3: next_state <= S0;
88     endcase
89 endcase
90
91 always @(state, IN)
92     case (state)
93         S0,S1,S2,S3,S4,S5: OUT <= NS;
94         S6: case (IN)
95             I0,I1,I2: OUT <= NS;
96             I3: OUT <= REL;
97         endcase
98         S7,S8: case (IN)
99             I0,I1,I2: OUT <= NS;
100             I3: OUT <= REF;
101         endcase
102         S9: case (IN)
103             I0,I1: OUT <= NS;
104             I2: OUT <= REL;
105             I3: OUT <= REF;
106         endcase
107         S10: case (IN)
108             I0: OUT <= NS;
109             I1: OUT <= REL;
110             I2,I3: OUT <= REF;
111         endcase
112     endcase
113 endmodule
114
```